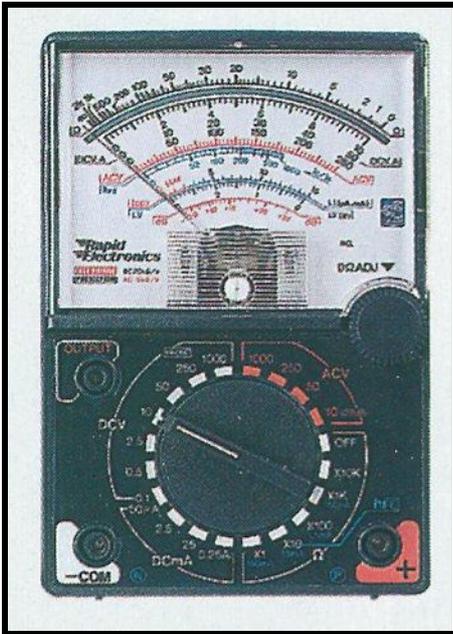


ELECTRONIC
PRODUCTS

REVISION
NOTES



MULTIMETERS



There are two main types of Multimeter, Analogue (shown left) and Digital (shown right). Digital meters are very accurate but analogue meters can show a slowly changing reading more clearly.


Multimeters have many functions but all can measure Voltage, Current and Resistance.

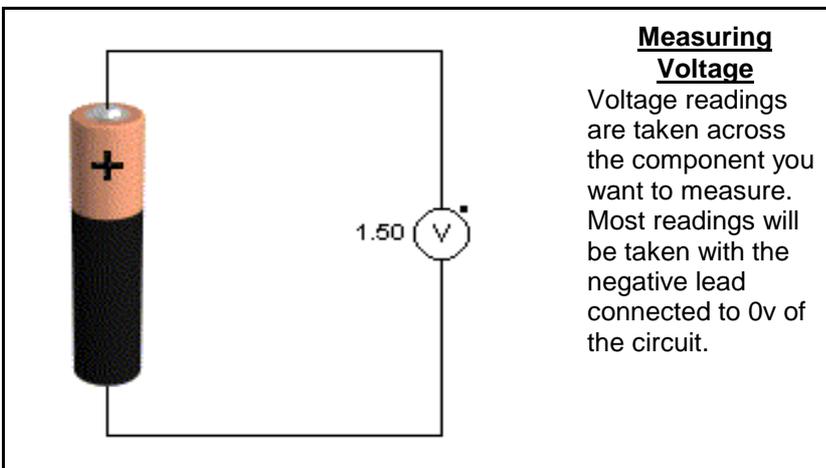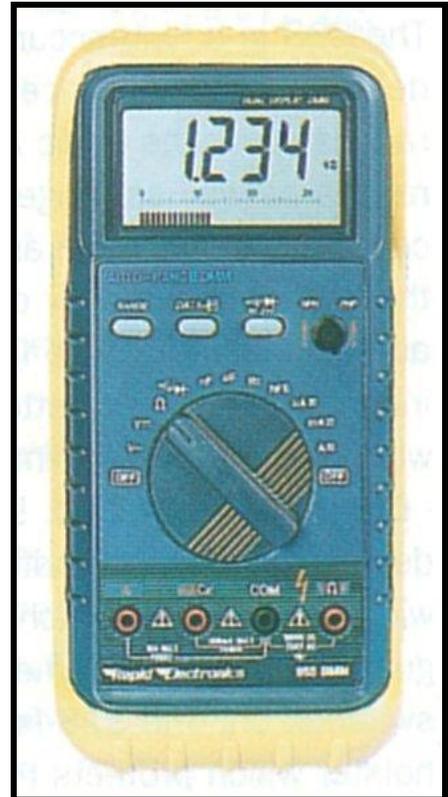When measuring unknown quantities, always set the meter to the highest range first and work your way down.



Measuring Voltage

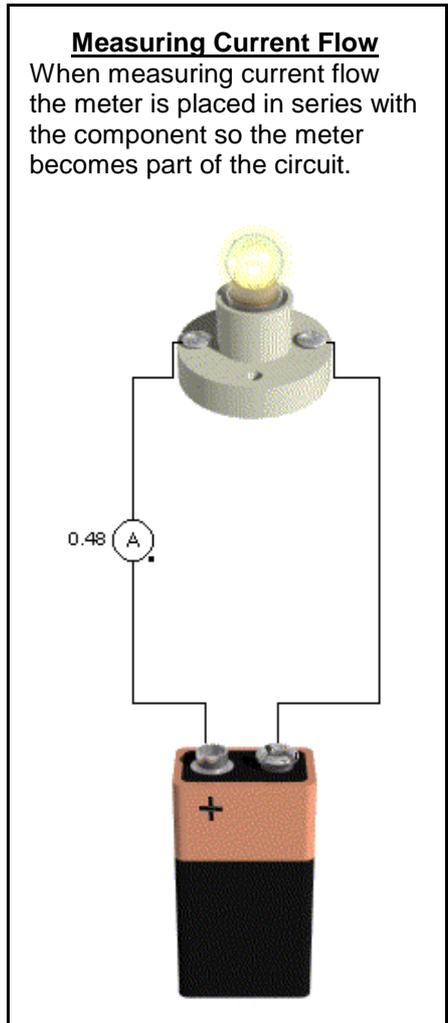Voltage readings are taken across the component you want to measure. Most readings will be taken with the negative lead connected to 0v of the circuit.



Measuring Current Flow

When measuring current flow the meter is placed in series with the component so the meter becomes part of the circuit.

Measuring Resistance or Continuity.



When measuring resistance you must disconnect any power and try to have one end of the component disconnected so that you get a true reading. You can also test for continuity or breaks in a wire or copper track. Select a low resistance range on the meter and put the probes on either end of the item you want to test. If the reading is 0.00 then there is continuity (closed circuit). If the display flashes a 1 then there is **no** continuity (open circuit).

CALCULATIONS


Resistor Colour Code

The first two bands represent the first two digits. The third band is the multiplier. An easy way to think of this is that the colour represents the number of zeros.

The fourth band states the tolerance, (how accurate the resistor is):

Red = 2 %
 Gold = 5 %
 Silver = 10 %

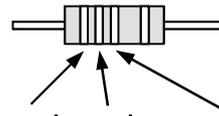
When gold is the third band then divide by 10
 When silver is the third band then divide by 100



Colour	1st	2nd	3rd band - no. of zeros
Black	0	0	none
Brown	1	1	0
Red	2	2	00
Orange	3	3	000
Yellow	4	4	0000
Green	5	5	00000
Blue	6	6	000000
Violet	7	7	
Grey	8	8	
White	9	9	
Gold			0. (divide by 10)
Silver			0.0 (divide by 100)


Ohms Law

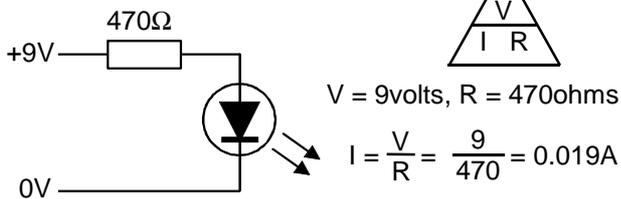The relationship between voltage, current and resistance is shown by Ohms Law:




Power Law

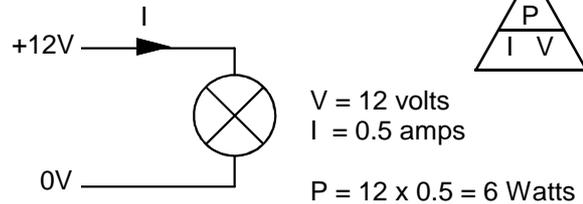The relationship between power, current and voltage is shown by the Power Law:




Combining Components


For two or more resistors in series

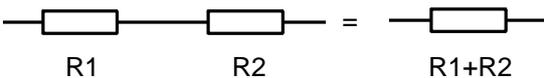


For two resistors in parallel

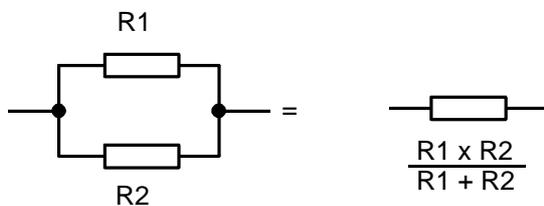


For three or more resistors in parallel

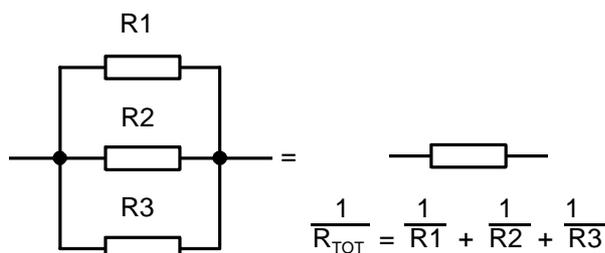


For two or more capacitors in parallel

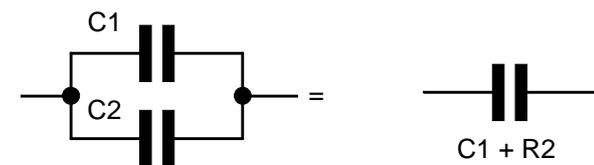

For two capacitors in series

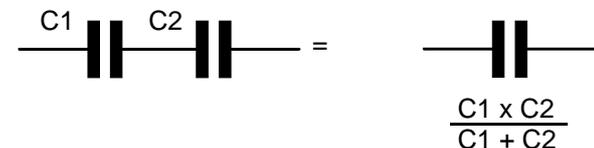


For three or more capacitors in series

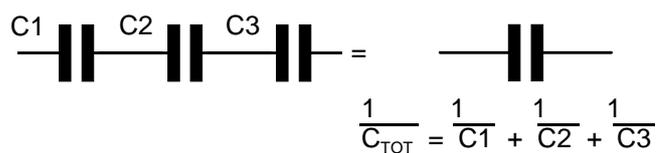


TRANSISTORS

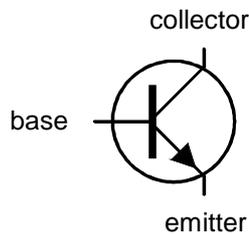The standard Bipolar transistor can be used as a switch or an amplifier, depending on how you connect to it. There are two polarities of bipolar transistor, NPN and PNP.




NPN bipolar transistor

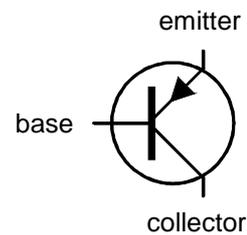

PNP bipolar transistor

Transistor Parameters

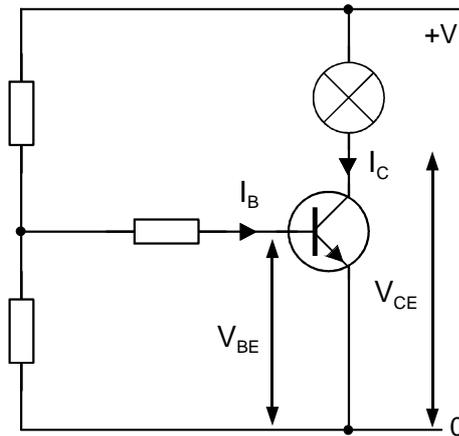

The diagram shows the basic current flow and voltages when a transistor is in use. These are called parameters.


- V_{BE} - The voltage between the base and emitter
- V_{CE} - The voltage between the collector and emitter. This is usually the maximum voltage the transistor can tolerate.
- I_C - The amount of current flowing into the collector
- I_B - The amount of current flowing into the base.
- h_{FE} - The current gain of the transistor = $\frac{I_C}{I_B}$

NOTE: V_{BE} must be 0.6v or more to turn on transistor.

Manufacture and Packaging

Below is an extract from a manufacturers catalogue showing the details of various transistors. Notice how the more you buy of one transistor, the cheaper each transistor becomes. N.B. Power = $P_{TOT} = I_C \times V_{CE}$

Transistor Number	Polarity	Case Style	I_C (max) mA	V_{CE} V	h_{FE} (min/max)	Power mW	Application	Price		
								1 - 24	25+	100+
BC107	NPN	TO18	100	45	110-450	300	Audio Driver	£0.24	£0.20	£0.18
BC108	NPN	TO18	100	20	110-800	300	General Purpose	£0.24	£0.20	£0.18
2N3904	NPN	TO92	200	40	100-300	350	Switching	£0.13	£0.10	£0.08
ZTX300	NPN	E-line	500	25	50-300	300	General Purpose	£0.17	£0.15	£0.12
2N3053	NPN	TO39	700	40	50-250	5000	General Purpose	£0.43	£0.33	£0.28
BFY51	NPN	TO39	1000	30	40 min.	800	General Purpose	£0.39	£0.31	£0.26
TIP31A	NPN	TO220	3000	60	25	40W	Audio Amp	£0.58	£0.51	£0.44
2N3055	NPN	TO3	15000	60	20 min.	115W	High Power Amp	£1.26	£0.96	£0.78
BC178	PNP	TO18	100	25	125-500	300	General Purpose	£0.28	£0.23	£0.17
BC559	PNP	TO92	100	30	240	500	Low noise amplifier	£0.10	£0.05	£0.04
ZTX500	PNP	E-line	500	25	50-300	300	General Purpose	£0.17	£0.13	£0.10
TIP122	NPN	TO220	5000	100	5000	65W	Hi-Power Darlington	£0.84	£0.60	£0.44
TIP127	PNP	TO220	10000	100	3000	125W	Hi-Power Darlington	£0.84	£0.60	£0.44

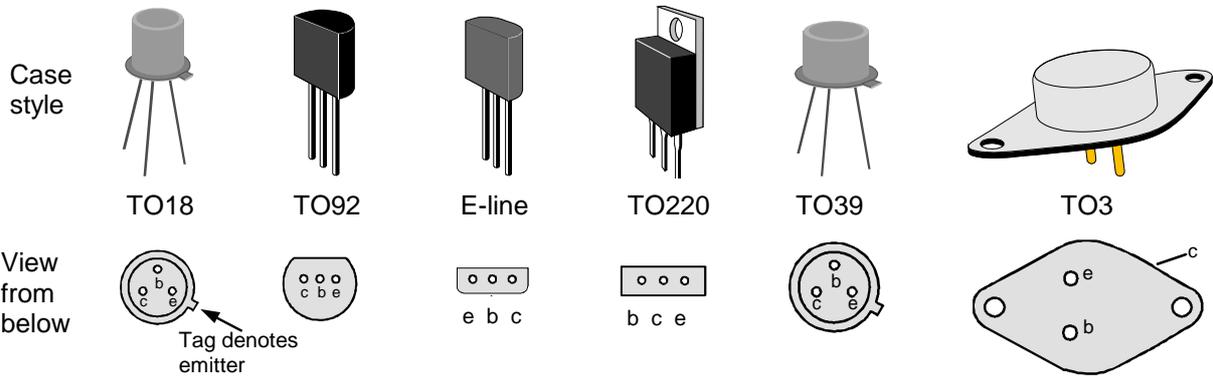


LOGIC GATES

Logic gates are components used to make decisions in circuits. The inputs can be connected to various sensors, and circuits can be designed to operate when certain conditions are met. When using logic, we refer to +v as a '1' and zero volts as a '0'. Each gate has its own rule it follows to produce an output.

Below is the most basic gate.

A circle on the output of the symbol will invert the output, but the action of the gate stays the same.


BUFFER gate

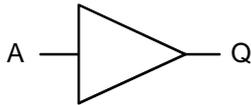

A	Q
0	0
1	1

Rule: Output is **on** if input is on.


NOT gate (INVERTER)

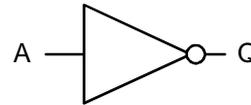

A	Q
0	1
1	0

Rule: Output is **off** if input is on.

OR gate

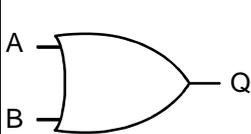


A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

Rule:
Output is **on** if A **OR** B are on

When a NOT gate is added to the output, the rule is the same but the output is the opposite - it is inverted.


NOR gate

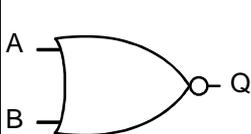

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

Rule:
Output is **off** if A **OR** B are on

AND gate

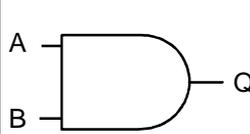


A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

Rule:
Output is **on** if A **AND** B are on

With a NOT gate added to the output, it becomes a


NAND gate

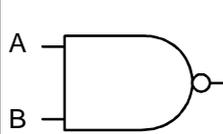

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

Rule:
Output is **off** if A **AND** B are on

EXCLUSIVE OR (XOR) gate

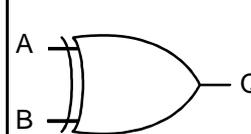


A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

Rule:
Output is **on** if A **OR** B are on but not both

With a NOT gate added to the output, it becomes an


EXCLUSIVE OR (XNOR) gate

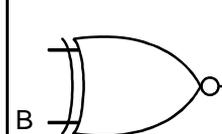


A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

Rule:
Output is **off** if A **OR** B are on but not both

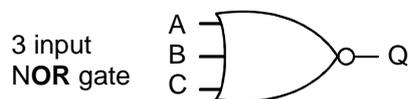All these gates can have 3, 4 and sometimes 8 or more inputs. The rules are exactly the same as for their 2 input version.




Output is **off** if A OR B OR C are on

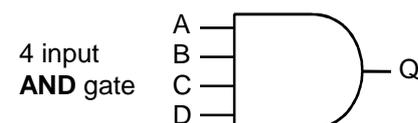

Logic gates can be combined to perform more complex tasks and decisions.


A common example is a **bistable** latch using two NOR gates, also known as a Set/Reset (S/R) flip-flop.

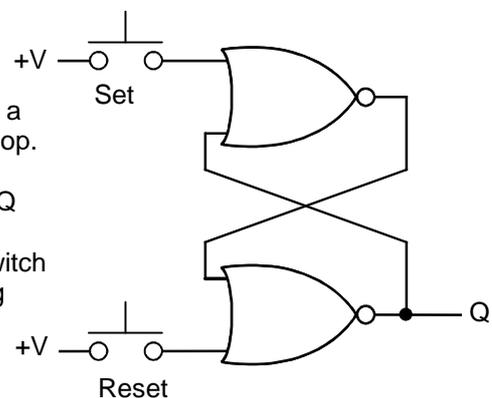Pressing Set makes Q go to 1 and remain in that state after the switch is released. Pressing Reset will make Q return to 0.



TIMING

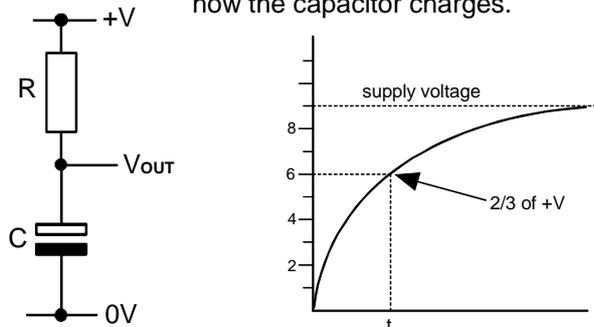Most timing circuits are based around a capacitor charging through a resistor. The graph shows how the capacitor charges.




The formula $t=CR$ is used to calculate the time it takes for the capacitor to charge to 2/3 of +V.


A common I.C. used for timing is called the **555** timer. It is housed in a standard 8 pin DIL (Dual In Line) package.



Notch shows top of I.C.


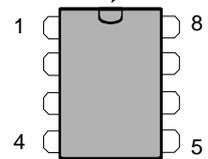


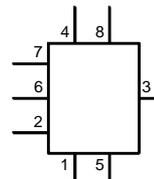Pin numbers are placed on the connections to the I.C. in circuit diagrams.




The Monostable

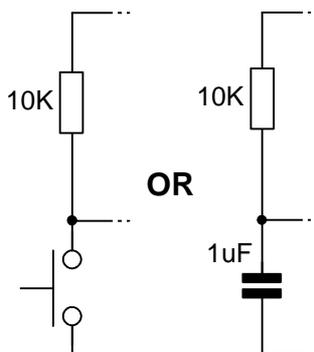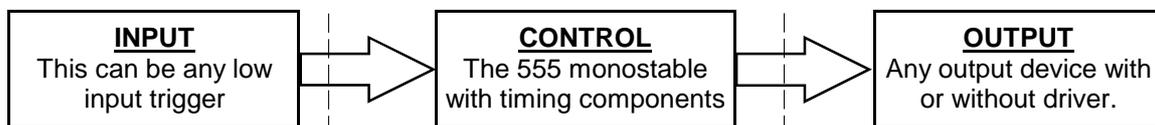
A monostable is a device that produces a single timed pulse that can control other devices, (mono meaning one). The input can be anything that produces an input from high to low. The output can provide about 50mA and can drive low current devices. A transistor driver is used to drive high current devices.



OR

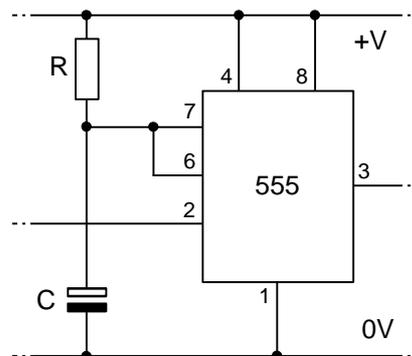

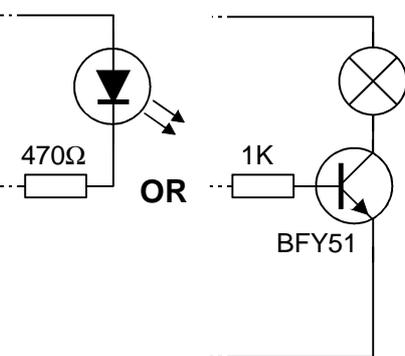The 555 timer can be connected as a monostable. The timing is set by R and C. The formula is $t = 1.1CR$



OR

A simple push-to-make switch with a pull-up resistor.

An RC circuit will produce a brief low pulse at power up.

The output can supply enough current to drive an LED.

For a light bulb output, a transistor driver is needed.


The Astable

An astable is a device that continually produces pulses at a certain rate known as its **frequency**. The 555 can also be connected as an astable. R2 can be a variable resistor so the frequency can be adjusted.

The frequency is determined by the following formula:

$$f = \frac{1.44}{(R1+2R2)C}$$

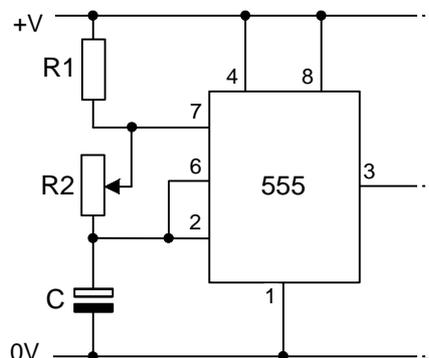The output can drive a low current device. Again a transistor or Darlington pair must be used to drive higher current devices.



The output is known as a **square wave** with equal **mark/space** ratio.




A speaker can be connected through a capacitor to produce an audible tone.


47uF

CIRCUIT SYMBOLS


INPUT DEVICES - SENSORS

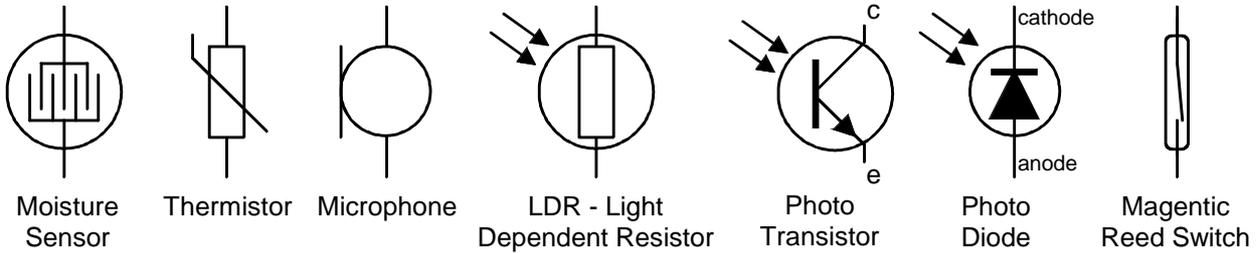


POWER AND MEASUREMENT

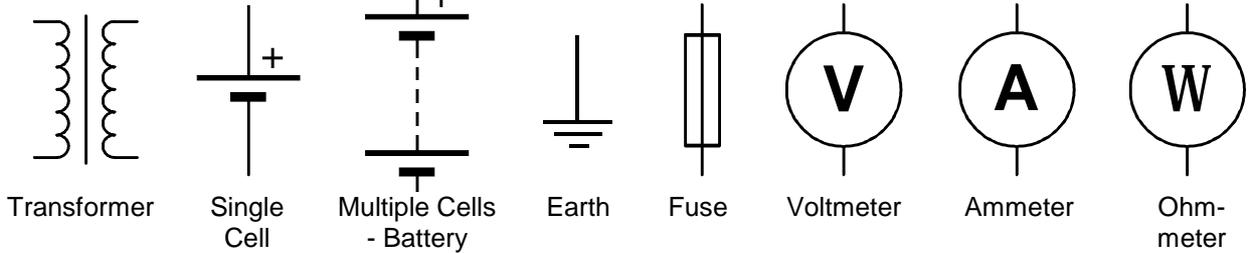


SEMI-CONDUCTORS

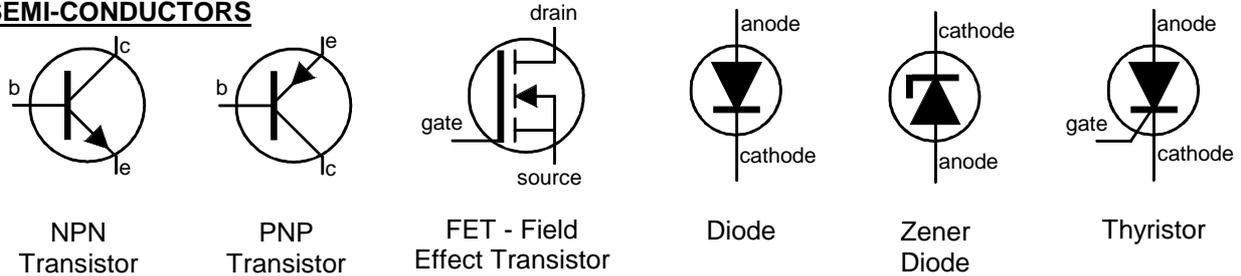


SWITCHES

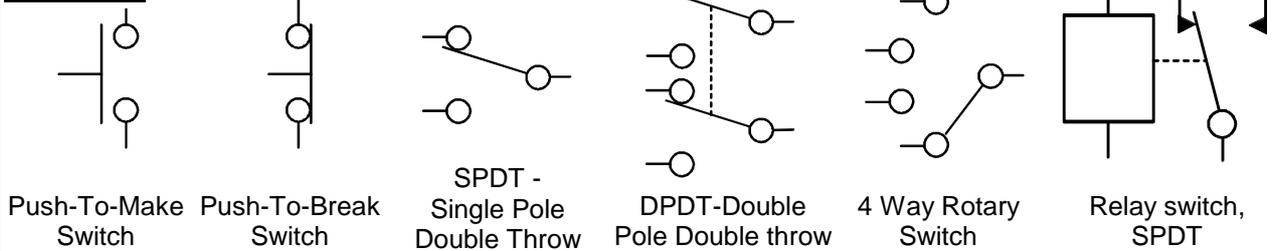


RESISTORS & CAPACITORS

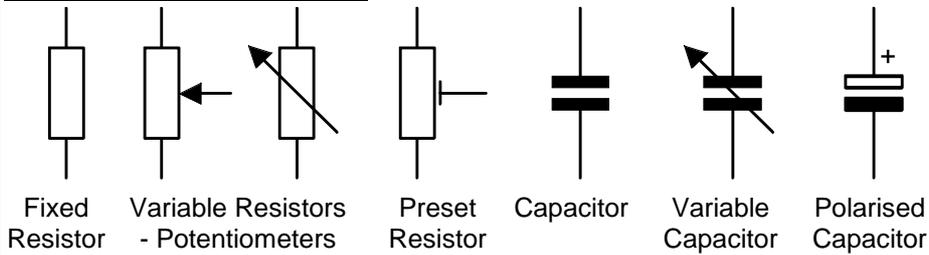


CONNECTIONS

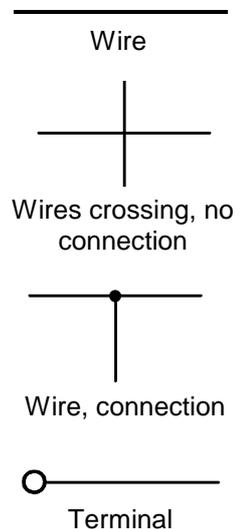

OUTPUT DEVICES

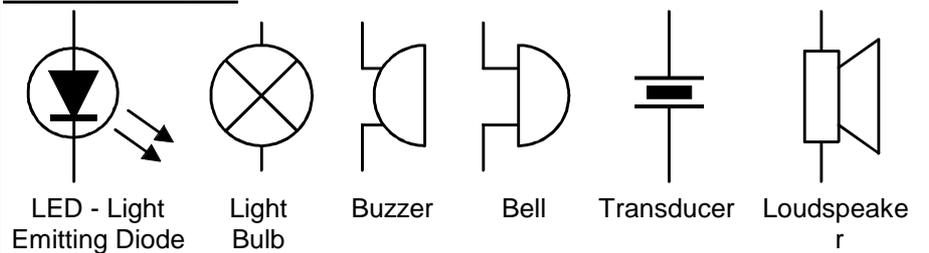

SENSING CIRCUITS

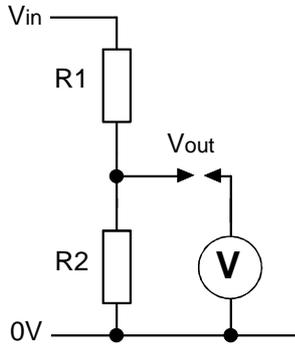


Voltage Dividers

A voltage divider is simply a way of connecting two resistances in series to produce a fraction of the input voltage. The output is at the junction of the two resistances and is determined by:

$$V_{out} = V_{in} \times \frac{R2}{R1 + R2}$$

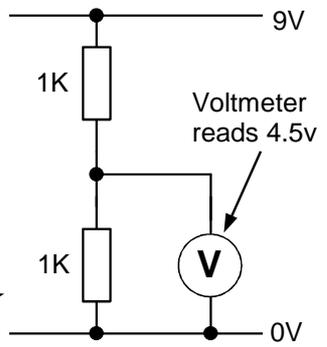TIP! If the two resistors are the same value, then the output will be exactly half the input.




9V

1K


1K

Voltmeter reads 4.5v

0V

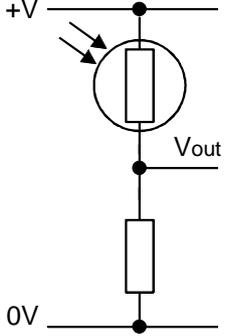


Light detector

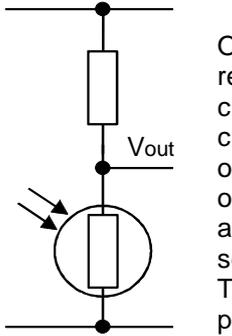


Dark detector

Sensing

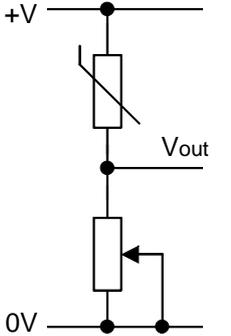
One of the resistances can be replaced with a sensor that changes its resistance. When a change in condition happens, the output voltage changes. The other resistor can be replaced by a variable resistor giving the sensor circuit some adjustment. These components can be placed in either order to produce the opposite change in output.



Heat detector

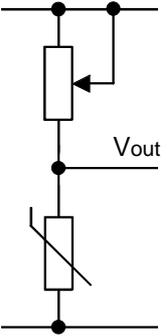


Frost detector

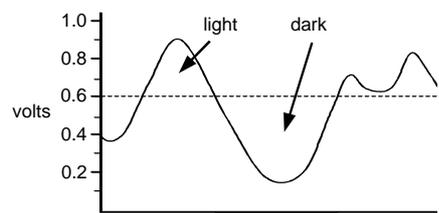

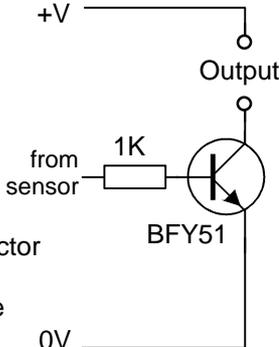1.0
0.8
0.6
0.4
0.2
volts

light dark

This is the output from a light detector circuit. The output voltage is constantly changing and cannot be used to drive any output devices.




+V

Output

from sensor 1K

BFY51

0V

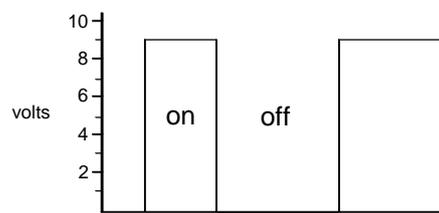

10
8
6
4
2
volts


on off

The output from the sensor can be connected to the base of a transistor as shown. When the input voltage rises above 0.6v, then the output is switched on.

Operational Amplifier

These devices have two inputs, **inverting** and **non-inverting**. The way they work is as follows. The difference between the voltages at the two inputs is amplified to the output by about 10,000 times! If V_I is greater than V_N then the output is negative. If V_I is less than V_N then the output is positive. If V_I equals V_N then the output is zero.

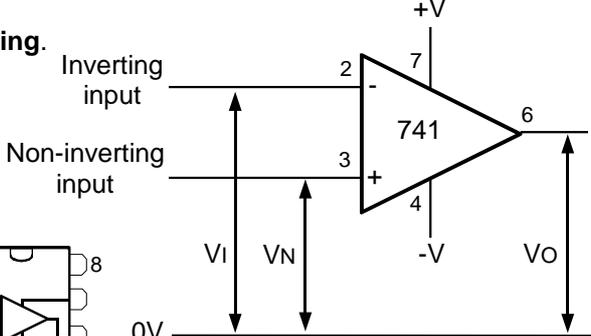They usually use **split power** supplies, (+V, 0V, -V) but can also be used with a normal battery.




Inverting input

Non-inverting input

741

V_I V_N V_O

8 pin DIL package of 741 device

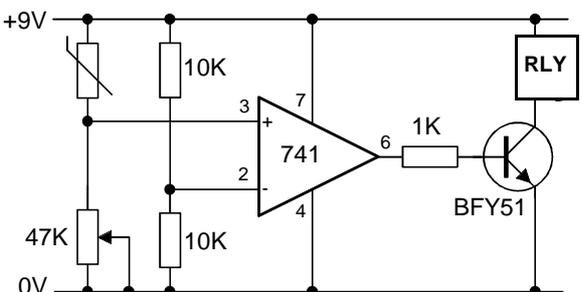

+9V

10K

3

7

741

4

10K

2

6

1K

RLY

BFY51

0V

47K


Here the operational amplifier has been used as a **comparator**. It compares between the input sensor voltage and a reference voltage from another voltage divider. The output switches a relay to operate a heater. When the heat rises the relay switches off until the temperature drops again, switching the heater back on. This is an example of **sensor feedback**.

DRIVING OUTPUTS


Relays

A relay is a device that can activate a switch using an electro-magnet. This is useful when devices need to be isolated from the control circuitry. For example a battery controlled temperature sensor could activate the relay which switches on a 240v mains fan.

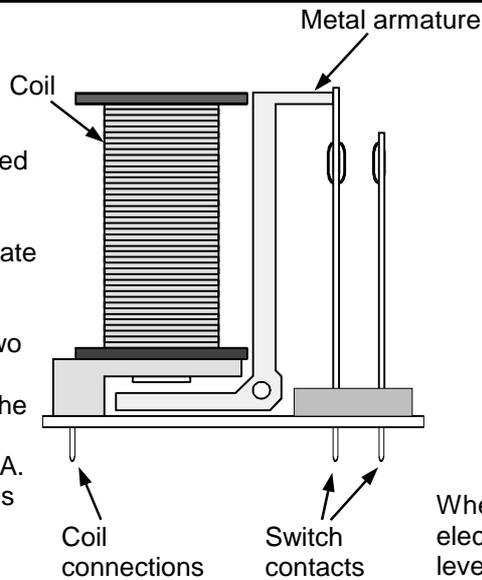The most basic type has just two contacts (SPST) that connect when the relay is **energised**. The coil is connected to the battery circuit and draws around 150mA. Some contacts can have ratings up to 16 Amps for car accessories.





Relay energised.

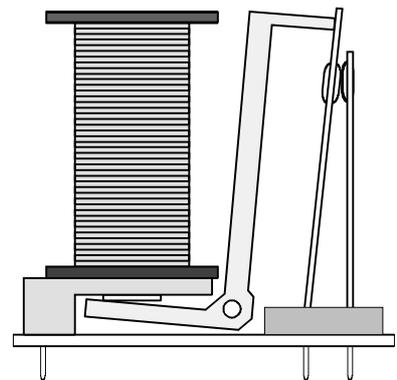

When energised, the coil becomes an electro magnet, attracting the metal lever, pushing the contacts together.

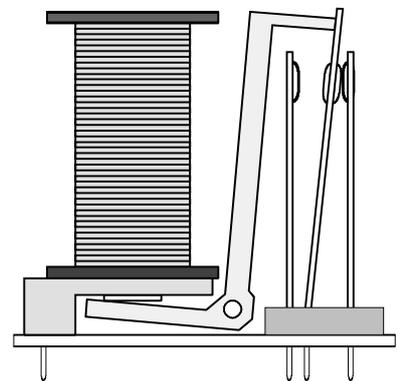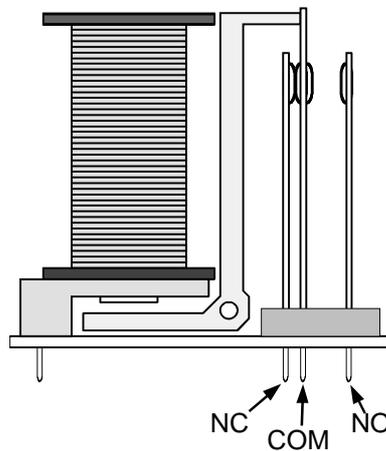Some relays have 3 contacts, (SPDT). When the relay is at rest, the **common** and **normally-closed** contacts connect. When the relay is energised, the common contact is pushed against the **normally-open** contact, forming a new connection. The diagrams show a single pole relay, meaning one set of contacts. Relays with 2, (DPDT), 3 and 4 poles are readily available



These contacts are sometimes known as changeover contacts.

Darlington Pair

Generally transistors have either high power capability, or high gain, but not both. To overcome this, two transistors can be connected together as shown to form a Darlington pair. The first transistor has high gain, the second has high current capability. The final gain is the product of the two.

eg.


T1 = BC108 - hfe = 400

T2 = TIP31 - hfe = 50

Overall gain =


$$400 \times 50 = 20,000$$

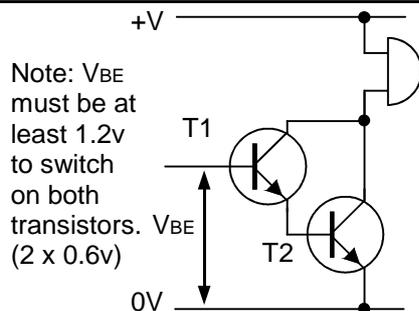The current capability is that of T2. Best of both worlds!



Note: V_{BE} must be at least 1.2v to switch on both transistors. ($2 \times 0.6v$)

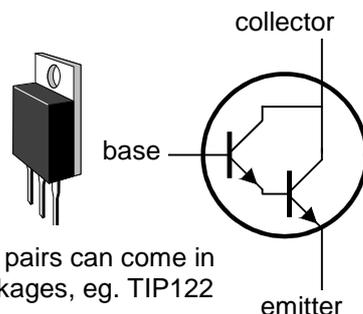
Two transistors wired as a Darlington Pair to drive a bell.



Darlington pairs can come in single packages, eg. TIP122

Thyristors

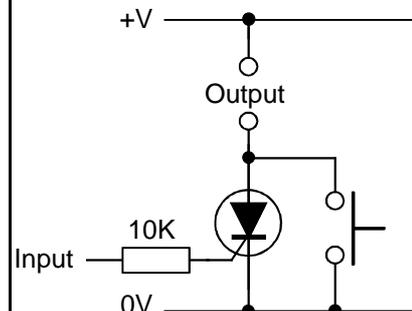Thyristors are a semi-conductor device that can switch on and latch output devices.



Once an input is sent to the gate, the thyristor conducts and latches on. The only way to switch off the output is either disconnect the power or short out the thyristor using a push switch. Some thyristors can switch up to 30 Amps.